

Homework 1 (Sim)

EE 321
February 2, 2020

Kevin Evans
ID: 11571810

- 2.77 (a) See attached sheet.
- (b) Plotting v_O/v_I , the average gain $A_V = 2.81$ (or 20 dB). See attached sheet with “Gain” plot.
- (c) The largest sine wave would be before saturation. If it saturates at ± 14 V, then the largest sine wave would be 28 V_{pp} or 4.95 V_{rms}.