```
L = 1.146e-3;
R_L = 2.23;
R 1 = 67.42;
R_2 = 1.20;
C = 9.59e-6;
R_S = 50;
A = [-1/(C*(R_S+R_1)) -1/C;
     1/L
                    -((R_2 + R_L)/L)];
B = [1/(C*(R S+R 1));
    0
                    ];
C = [1 0;
    0 1];
D = [0;
    0];
sys = ss(A,B,C,D);
[Y,T,X] = step(sys);
subplot(2, 2, 1);
plot(T, 10*X(:, 1));
xlabel('time [s]');
ylabel('x_1(t) [V]');
grid on;
subplot(2, 2, 3);
plot(T, 10*X(:, 2));
xlabel('time [s]');
ylabel('x 2(t) [A]');
grid on;
subplot(2, 2, [2, 4]);
plot(10*X(:,1), 10*X(:,2));
xlabel('x_1(t) [V]');
ylabel('x 2(t) [A]');
grid on;
```